

Three-phase Circuits

Homework

1. Solve for the line currents in the Y- Δ circuit of Fig.1. Take $Z_{\Delta} = 60 \angle 45^{\circ} \Omega$.

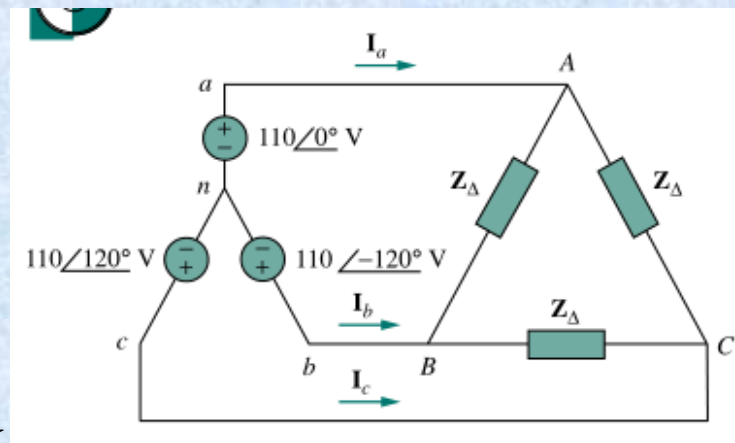


Figure 1

$$\mathbf{V}_{AB} = 110 \angle 0^{\circ} - 110 \angle -120^{\circ} = 110\sqrt{3} \angle 30^{\circ} \text{ V}$$


$$\mathbf{V}_{BC} = 110 \angle -120^{\circ} - 110 \angle 120^{\circ} = 110\sqrt{3} \angle -90^{\circ} \text{ V}$$

$$\mathbf{V}_{CA} = 110 \angle 120^{\circ} - 110 \angle 0^{\circ} = 110\sqrt{3} \angle 150^{\circ} \text{ V}$$

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{Z_{\Delta}} = \frac{110\sqrt{3} \angle 30^{\circ}}{60 \angle 45^{\circ}} \approx 3.175 \angle -15^{\circ} \text{ A}$$

$$\mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{Z_{\Delta}} \approx 3.175 \angle -135^{\circ} \text{ A}$$
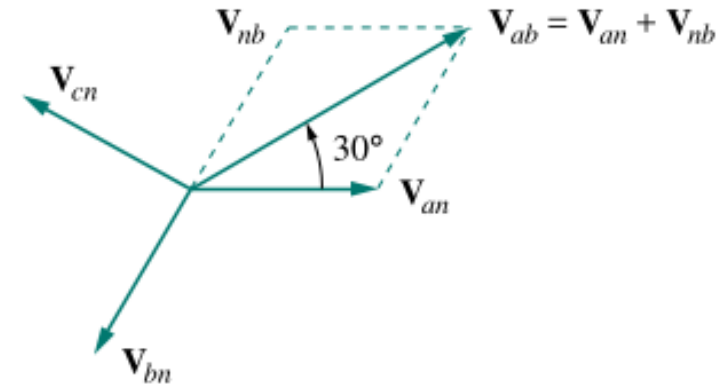
$$\mathbf{I}_{CA} = \frac{\mathbf{V}_{CA}}{Z_{\Delta}} \approx 3.175 \angle 105^{\circ} \text{ A}$$



$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA} = 3.175 (\angle -15^{\circ} - \angle 105^{\circ})$$

$$= 3.175\sqrt{3} \angle -45^{\circ} = 5.5 \angle -45^{\circ} \text{ A}$$

$$\mathbf{I}_b = 5.5 \angle -165^{\circ} \text{ A} \quad \mathbf{I}_c = 5.5 \angle 75^{\circ} \text{ A}$$

$$Z_{\Delta} = 60 \angle 45^{\circ} \Omega$$

$$Z_Y = Z_{\Delta} / 3 = 20 \angle 45^{\circ} \Omega$$

$$\mathbf{I}_a = \frac{110 \angle 0^{\circ}}{20 \angle 45^{\circ}} = 5.5 \angle -45^{\circ} \text{ A}$$



(3.89-j3.89)

$$\mathbf{I}_b = \frac{110 \angle -120^{\circ}}{20 \angle 45^{\circ}} = 5.5 \angle -165^{\circ} \text{ A}$$

(-5.31-j1.42)

$$\mathbf{I}_c = \frac{110 \angle 120^{\circ}}{20 \angle 45^{\circ}} = 5.5 \angle 75^{\circ} \text{ A}$$

(1.42+j5.31)

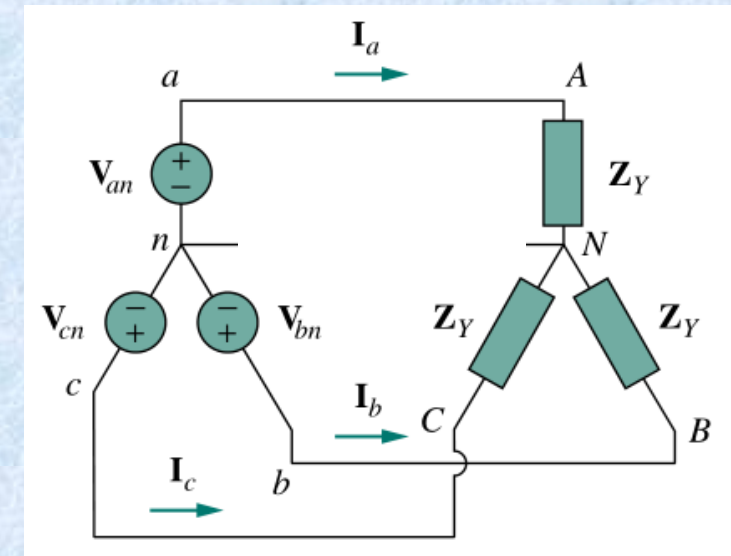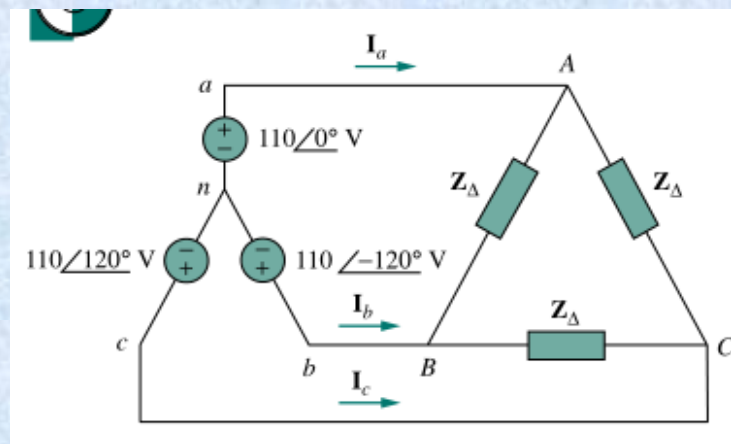

2. Obtain the line currents in the three-phase circuit of Fig.2.

$$Z = 6 - j8 = 10 \angle -53.13^\circ \Omega$$

$$I_a = \frac{440 \angle 0^\circ}{10 \angle -53.13^\circ} = 44 \angle 53.13^\circ \text{ A}$$

$$(26.4 + j35.2)$$

$$I_b = \frac{440 \angle -120^\circ}{10 \angle -53.13^\circ} = 44 \angle -66.87^\circ \text{ A}$$

$$(17.28 - j40.46)$$

$$I_c = \frac{440 \angle 120^\circ}{10 \angle -53.13^\circ} = 44 \angle 173.13^\circ \text{ A}$$

$$(-43.68 + j5.26)$$

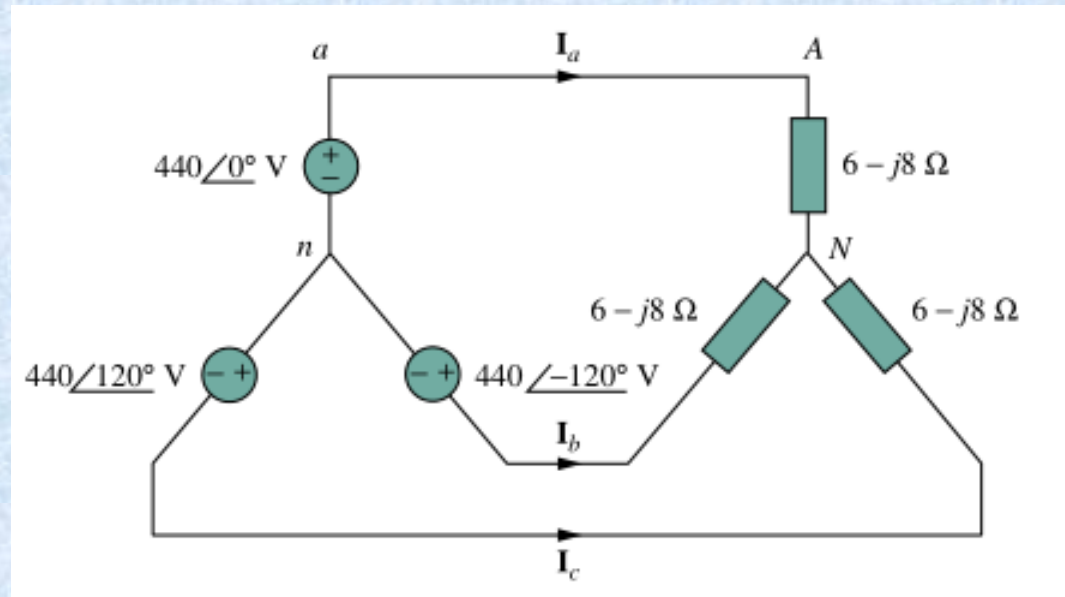


Figure 2

3. For the three-phase circuit in Fig. 3, find the average power absorbed by the delta-connected load with $Z_{\Delta} = 21 + j24\Omega$.

$$Z_Y = Z_{\Delta} / 3 + 1 + j0.5 = 8 + j8.5 \Omega$$

$$= 11.67 \angle 46.74^{\circ} \Omega$$

$$I_a = \frac{100 \angle 0^{\circ}}{11.67 \angle 46.74^{\circ}} \approx 8.57 \angle -46.74^{\circ} \text{ A}$$

$$P_a = 7 I_a^2 = 7 \times 8.57^2 = 513.76 \text{ W}$$

$$P = 3 P_a = 1541.28 \text{ W}$$

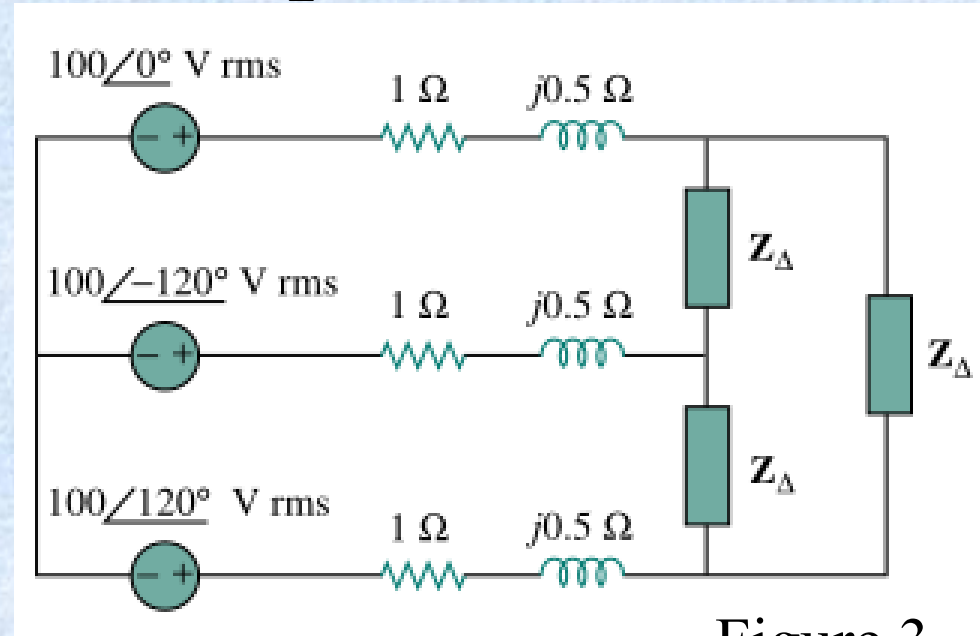


Figure 3

