

Problem 3

1. Obtain the transfer function $H(\omega) = I_o/I_s$ of the circuits shown in Fig. 1.

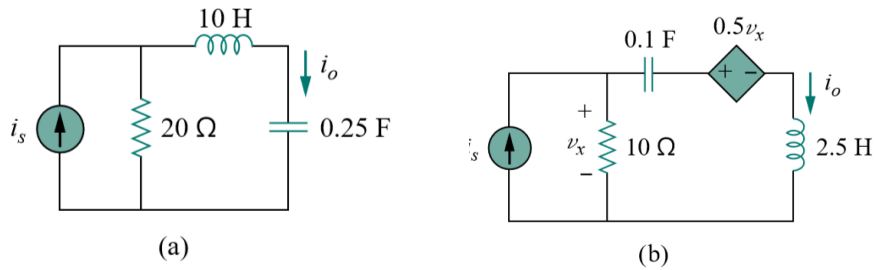


Figure 1

2. Find the transfer function $H(\omega) = V_o/V_i$ of the circuits shown in Fig.2.

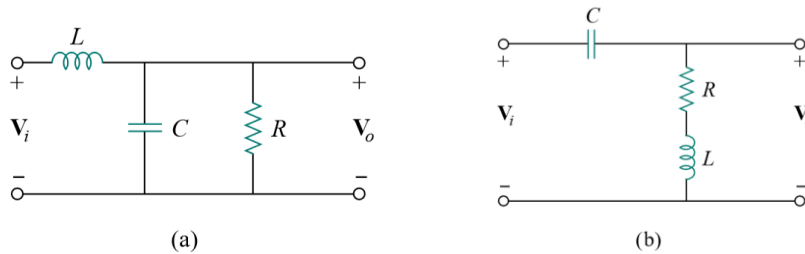


Figure 2

3. The RC circuit in Fig. 3 is used for a lead compensator in a system design. Obtain the transfer function of the circuit.

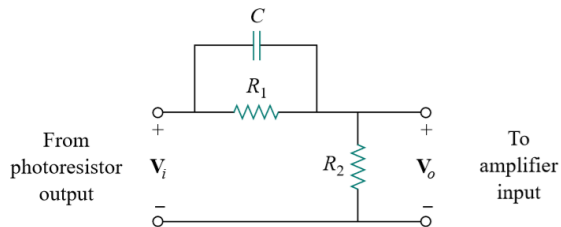


Figure 3

4. Draw the Bode plots for

$$H(\omega) = \frac{50(j\omega + 1)}{j\omega(-\omega^2 + 10j\omega + 25)}$$

5. Find the transfer function V_o/V_s of the circuit in Fig. 5. Show that the circuit is a lowpass filter.

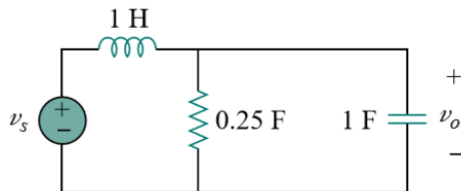


Figure 5

6. In a highpass RL filter with a cutoff frequency of 100 kHz, $L = 40$ mH. Find R .
7. Determine the center frequency and bandwidth of the bandpass filters in Fig. 7.

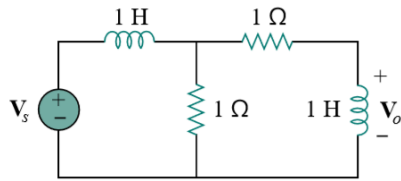


Figure 7

8. The crossover circuit in Fig. 8 is a lowpass filter that is connected to a woofer. Find the transfer function $H(\omega) = V_o(\omega)/V_i(\omega)$.

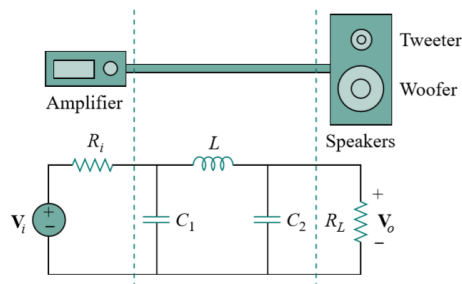


Figure 8

9. The crossover circuit in Fig. 9 is a highpass filter that is connected to a tweeter. Determine the transfer function $H(\omega) = V_o(\omega)/V_i(\omega)$.

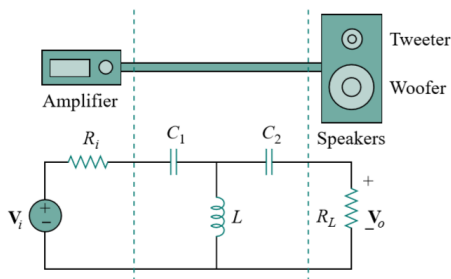


Figure 9

10. Design a series RLC type bandpass filter with cutoff frequencies of 10 kHz and 11 kHz. Assuming $C = 80$ pF, find R , L , and Q .
11. Obtain the transfer function of the active filter in Fig. 11. What kind of filter is it?

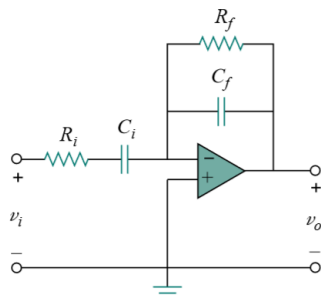


Figure 11

12. In an amplifier circuit, a simple RC highpass filter is needed to block the dc component while passing the time-varying component. If the desired rolloff frequency is 15 Hz and $C = 10 \mu\text{F}$, design the circuit and find the value of R .

13. A highpass filter is shown in Fig. 13. Show that the transfer function is

$$H(\omega) = \left(1 + \frac{R_f}{R_i}\right) \frac{j\omega RC}{1 + j\omega RC}$$

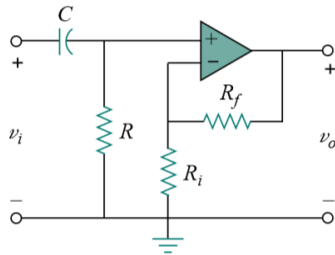


Figure 13

14. A second-order active filter known as a Butterworth filter is shown in Fig. 14.

(a) Find the transfer function V_o/V_i .

(b) Show that it is a lowpass filter.

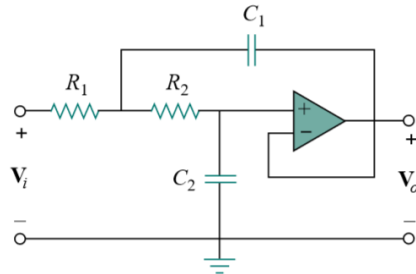


Figure 14

15. Calculate the resonant frequency of each of the circuits in Fig.15.

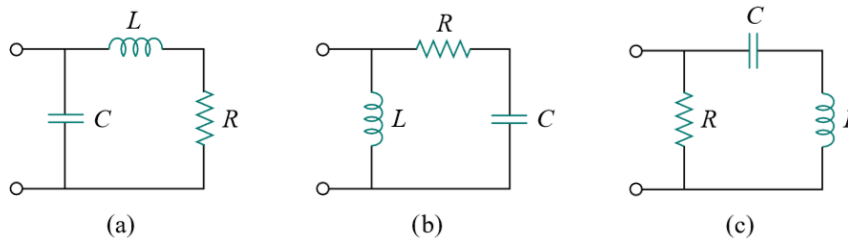


Figure 15

16. In an electronic device, a series circuit is employed that has a resistance of 100Ω , a capacitive reactance of $5 \text{ k}\Omega$, and an inductive reactance of 300Ω when used at 2 MHz. Find the resonant frequency and bandwidth of the circuit.

17. It is expected that a parallel RLC resonant circuit has a midband admittance of $25 \times 10^{-3} \text{ S}$, quality factor of 80, and a resonant frequency of 200 k rad/s . Calculate the values of R , L , and C . Find the bandwidth and the half-power frequencies.

18. For the network illustrated in Fig. 18, find

- the transfer function $H(\omega) = V_o(\omega)/I(\omega)$,
- the magnitude of H at $\omega_0 = 1 \text{ rad/s}$.

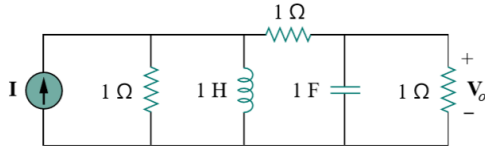


Figure 18

19. The dotted portion in the circuit shown in Fig.19 is the equivalent circuit of a practical inductor. V_1 and V_2 are AC voltmeters. When the frequency of the voltage source is adjusted to $f=900\text{kHz}$, voltmeter V_2 shows the maximum value and $V_1=1\text{mV}$, $V_2=62\text{mV}$. Given $C=200\text{pF}$, find L and r .


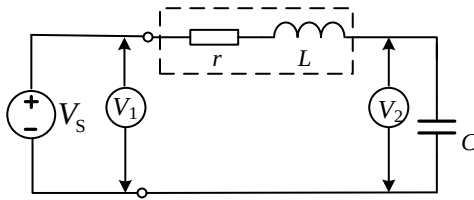



Figure 19

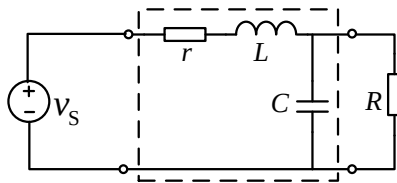20. In the series resonant circuit shown in Fig. 20(between the four little circles), given characteristic impedance $\rho = 1\text{k}\Omega$, there is no loss in capacitor. The inductor has an equivalent loss resistance r and its quality factor is $Q_L=100$. The resonant angular frequency is 100k rad/s . $R=50\text{k}\Omega$ is the load connected to the circuit.

- Find the quality factor Q of the circuit, bandwidth, L and C ;
- If the maximum value of V_s is 1V , considering the possibility of load R 's disconnection to the circuit, find the minimum withstand voltage for the capacitor C .
(电容的最小耐压值。当电阻 R 断开时，电路品质因数 Q 大幅升高，电容电压大幅上升，需具有一定的耐压)



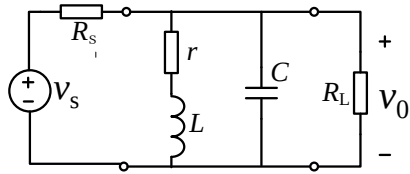21. The equivalent circuit of an intermediate frequency amplifier is shown in Figure21. Given the internal resistance of the source $R_s=150\text{k}\Omega$, inductance $L=590\mu\text{H}$, resistance $r=14.3\Omega$, capacitance $C=200\text{pF}$ and its loss neglected, and the equivalent load resistance $R_L=500\text{k}\Omega$, find the resonant frequency and the bandwidth.



22. In the circuit shown in Fig.22, given $r = 20\Omega$, $L = 10\text{mH}$,

- (1) Using the concepts of series resonance and parallel resonance, determine C_1 and C_2 so that when input v_s works in 100kHz , the output v_o is zero and when v_s works in 50kHz , the output v_o is maximum;
- (2) Determine the transfer function $H(j\omega)$ and find the frequencies at which $|H(j\omega)|=0$ and $|H(j\omega)|=1$, respectively, so that the conclusion can prove the results above.

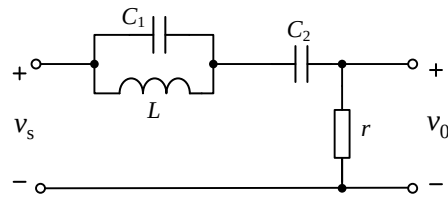


Figure 22